## Designer's casebook

## Ramp generator has separate slope and frequency controls

by Henrique S. Malvar Department of Electrical Engineering, University of Brazilia, Brazil

Isolating with four analog switches the frequency-determining portion of the circuit from that controlling the charging and discharging of its RC integrator, this ramp generator achieves independent selection of slope ratio and repetition rate. Such a unit is useful in a music synthesizer, where timbre must be changed without affecting a note's fundamental frequency.

Analog gates  $T_1$  and  $T_2$  are initially switched on, and therefore  $V_c$  is applied via operational amplifier  $A_1$  to the integrator built around  $A_2$  (see figure). Thus,  $-V_c$ 


appears at the inverting input of  $A_2$ , and its positivegoing output reaches voltage  $V_H$  in  $T_1 = 2V_HC$  $(R_1+R_2)/V_c$  seconds, where  $V_H = V_{cc}R_5/R_6$ .

At this time,  $A_3$  switches on and  $A_4$  goes off.  $T_1$  and  $T_2$  are thus disabled, and  $T_3$  and  $T_4$  are brought high so that  $+V_c$  is applied to the integrator. The output at  $A_2$  thus falls linearly toward  $-V_H$ , where time  $T_2 = 2V_HC(R_3+R_4)/V_c$ .

The frequency of the ramp is given by:

$$f = 1/(T_1 + T_2)$$
  
=  $R_6V_c/[2CR_5V_{cc}(R_1 + R_2 + R_3 + R_4)] = kV_c$ 

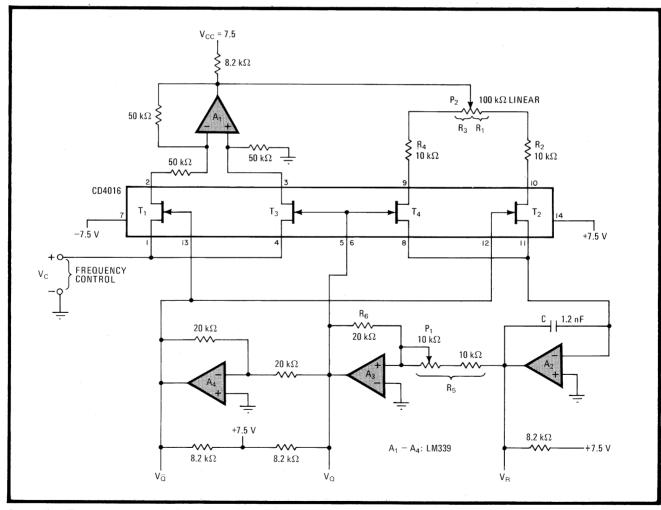where k is a constant (in the approximate range of 1 kHz/V) that can be adjusted with potentiometer  $P_1$ . Because  $R_1 + R_3$  is a constant, it is seen that an adjustment in potentiometer  $P_2$  will affect the slope ratio, but not the frequency. With the values shown, the slope ratio can be selected from 1/11 to 11. The slope ratio is given by  $T_1/T_2 = (R_1 + R_2)/(R_3 + R_4)$ .



**Separation.** Transmission gates  $T_1 - T_4$  separate the portion of the ramp generator that determines the frequency from the circuitry that sets the charge and discharge times of its integrator, so that the up/down slope ratio and frequency can be independently selected. The inexpensive circuit, which costs less than \$10 and works in the audio range, is a useful timbre control in music synthesizers.